

BERKE KUZHEY ARDIÇ

22103340

SECTION-004

## Detailed Explanation Of Design


In my implementation I first sketch the HLSM logic of the transmitter and receiver for the stage 1 of the project. Then I detailed the FSM and the datapath to recognize the logic and began to code. My transmitter FSM consisted of 8 states later in stage 3 I made it 9 these were two stop states that send stop bits, an init state, a wait state for button d, a load state, another wait for button c, counter and register clear state and counting and shifting states. The Transmitter logic was initializing a register, shift register and counter first then loading the data into the register and by using the shift register and counting up to the 8 sending data bit to bit to the receiver module. Meanwhile I was sending the necessary tx with a 4 to 1 mux to indicate receiver the process. The receiver FSM consisted of 5 states, logic was waiting for rx to be 0 and when rx is 0 take the data into a shift register and in the last stage load the data into the output register. In the coding stage first I designed the side modules that I will use into the main logic like eight-bit register, shift register, multiplexers, counter, baud rate generator. Then I implement two main modules: transmitter\_fsm and receiver\_fsm. In transmitter\_fsm it creates a 32 bit register that consists of 4 eight-bit data called txbuf a register called t register the handle the load to the shift register which is connected to the least significant 8 bits of the txbuf register. In state 0 I reset all the registers and counters. In State1 I wait for the button D and if button d is pressed I move on to the nextstate which is S2. In S2 after button D I load the data into the txbuf register of the transmitter module by taking the data into the most significant eight-bits and I shift the and move on to the nextstate to wait for the Button C. In S3 I wait for the Button C to be pressed and if button C is pressed I move on to the preparation state for the shifting stage then I shift the data and send

it with the tx. In the receiver logic is very simple I have an another array which will be used for the storing the send data when tx is 0 for the first time it moves to the receive state takes the data bit to bit into the shift register than connects it to the another eight-bit register and this eightbit register load the data to the most significant bits of the 32 bit register and while loading it shifts the register data to display the oldest 4 in a fifo structure.


In an another module called seven segment display I handle the seven segment display logic I take the rxbuf and the txbuf arrays as inputs for this module and create a 32 bit register and load it with rxbuf or txbuf by the input of button U and display the necessary bits regarding the button left and right. If the input is positive RorTx output in the module indicates and it also acts a decessor to understand which to display I handle this logic by simple if cases and I designed a digit for each anothe and kathode values to show the necessary digits.

## RTL SCHEMATICS

### UART

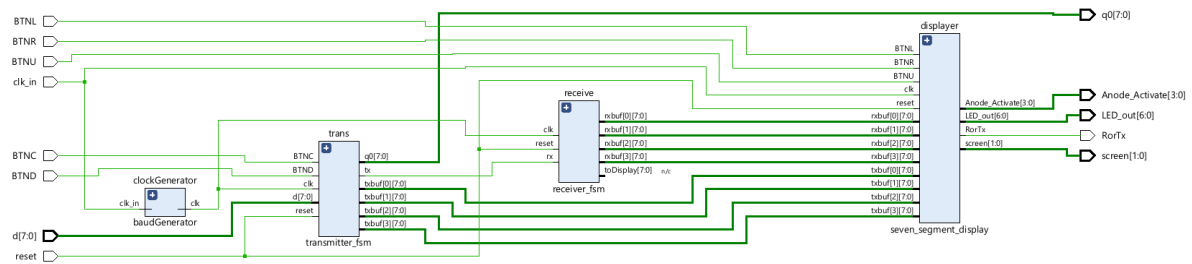


### Seven Segment Displayer

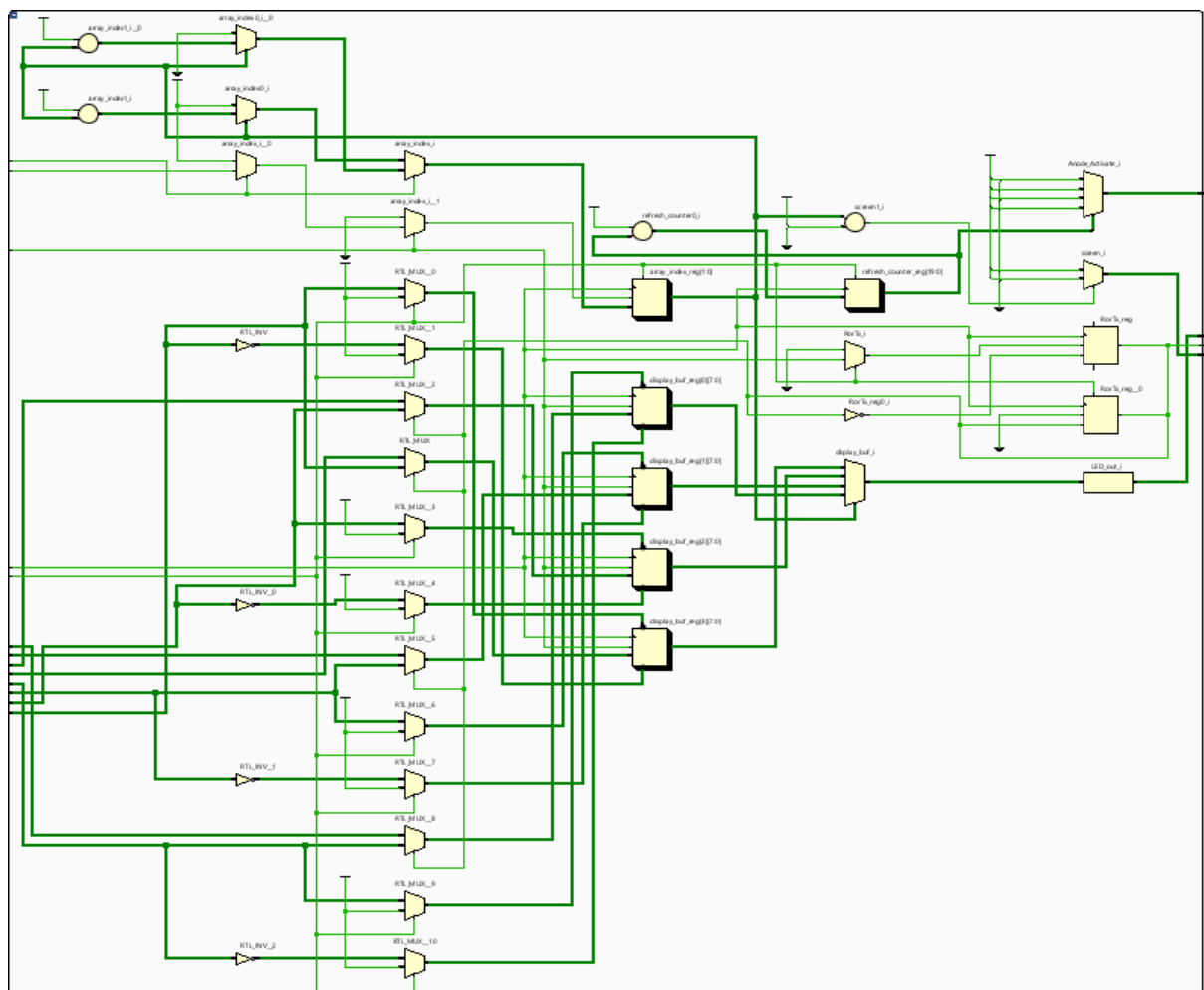


[illegible]


## Receiver

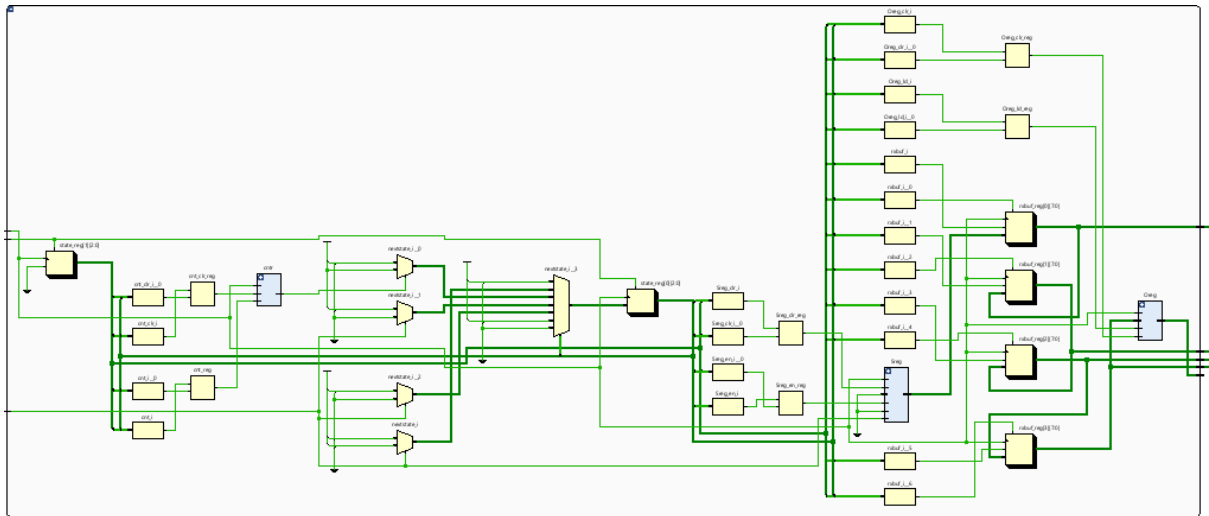

## State Diagrams

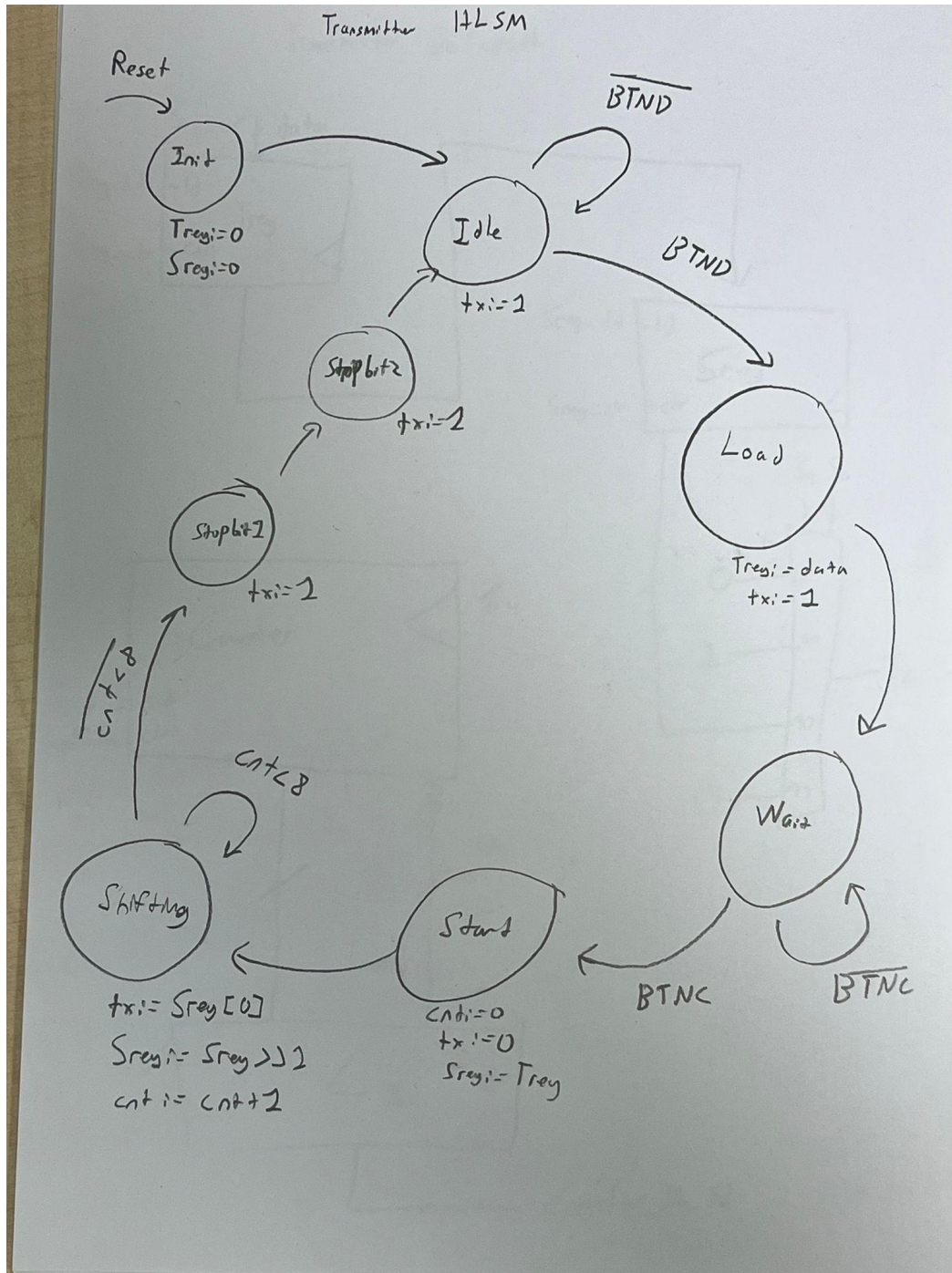




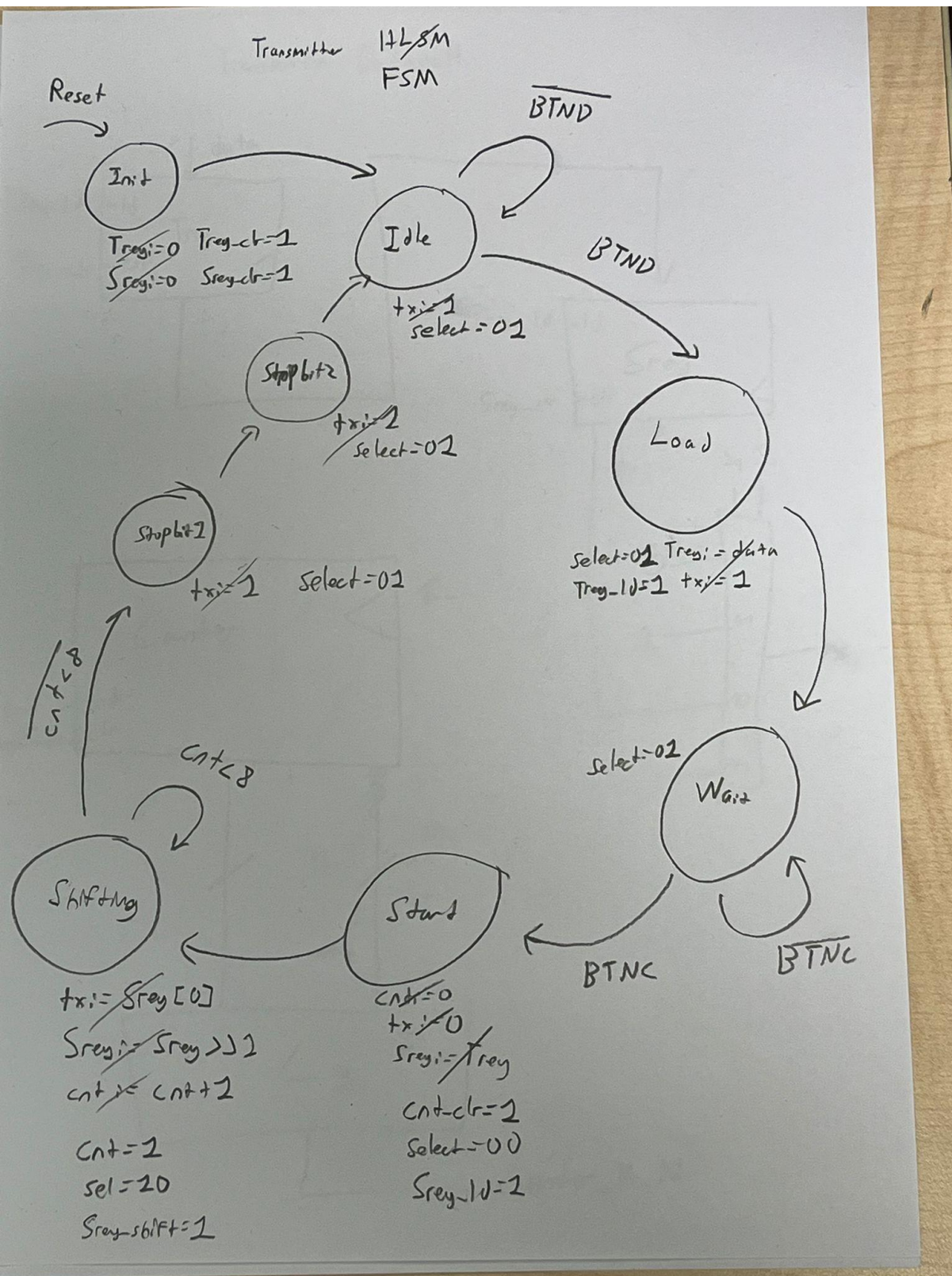




# Transmitter Datapath

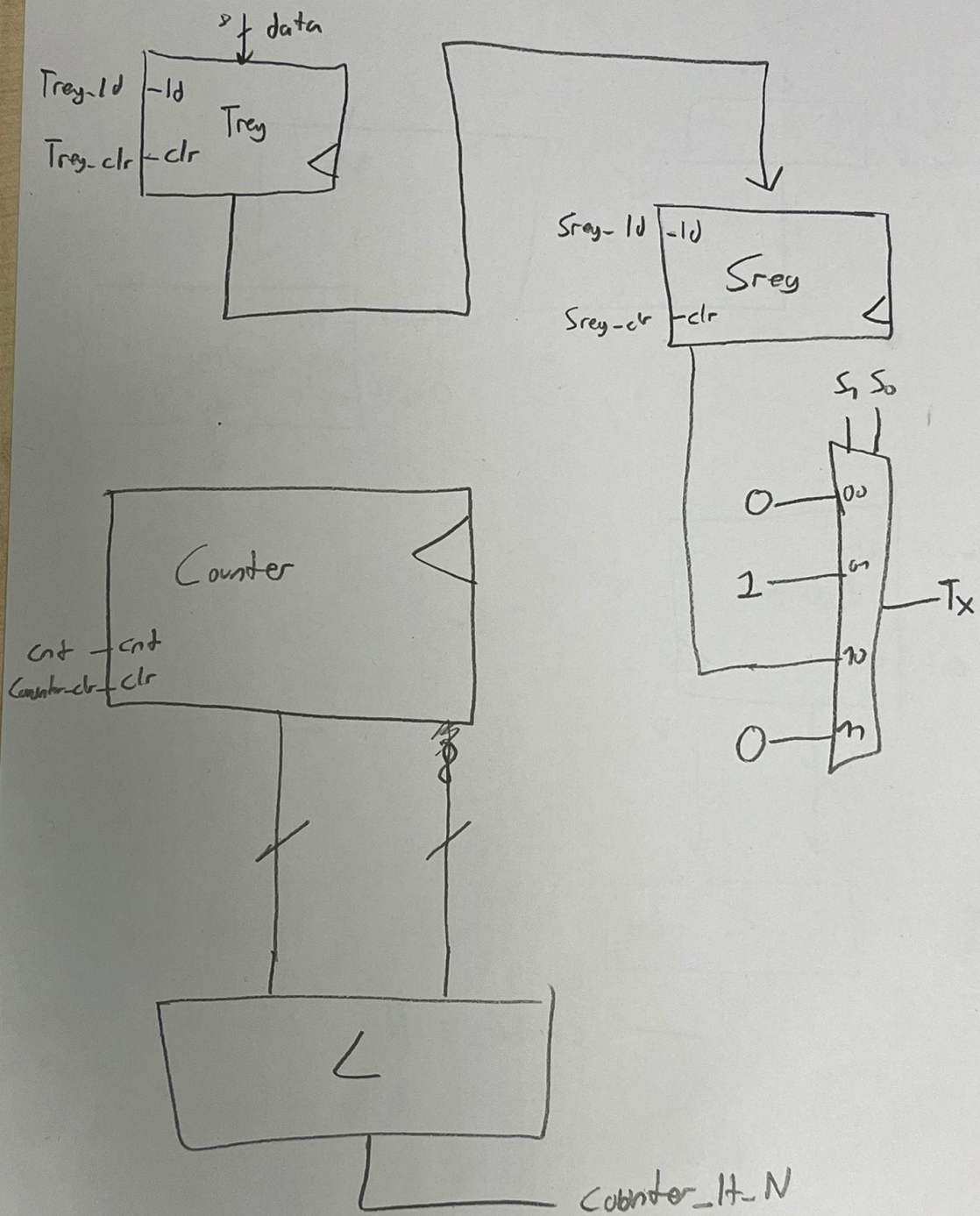


# Seven Segment Display I+LSM

 




# Receiver HFSM FSM

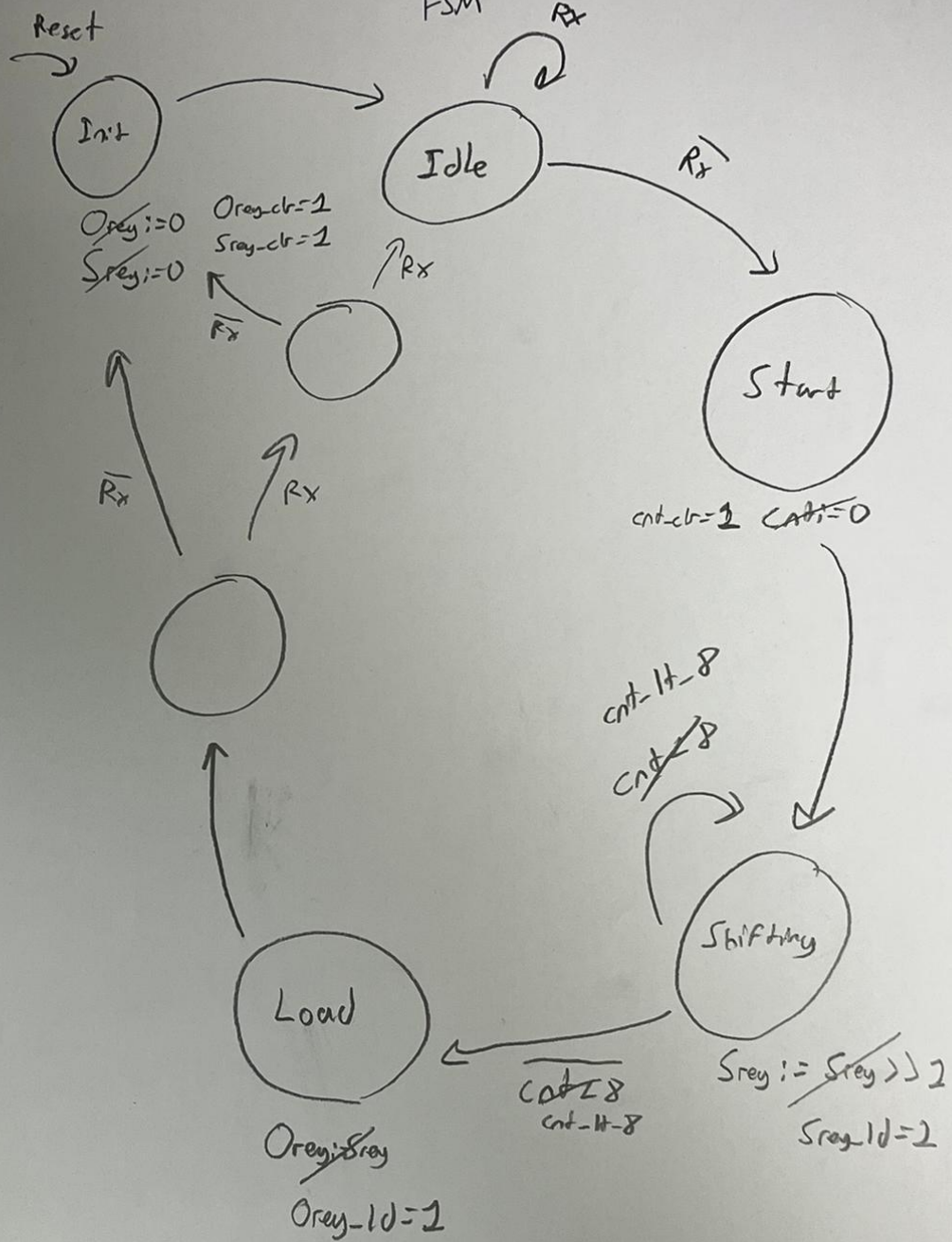


# Receiver HLSM

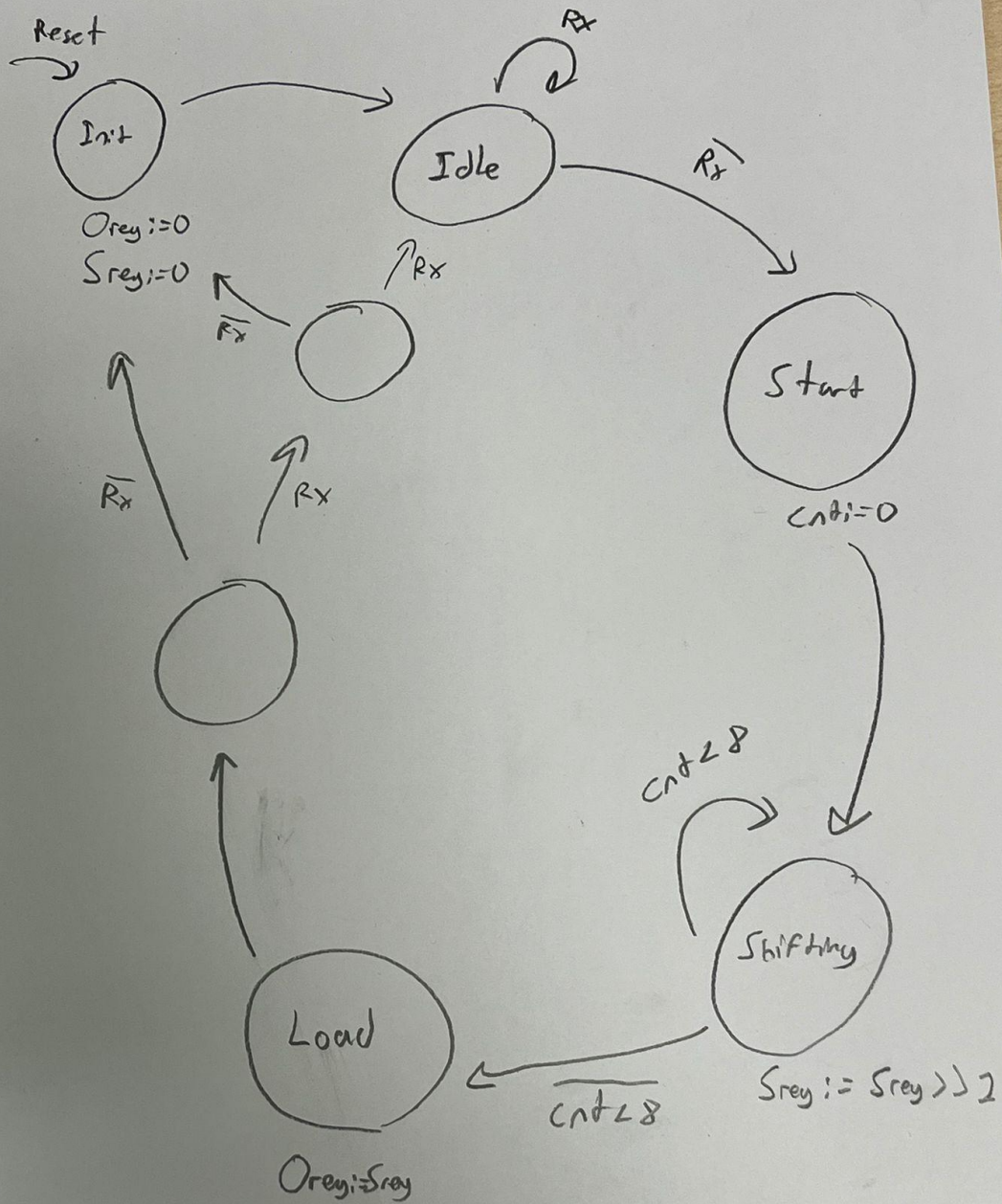



# Receiver Datapath

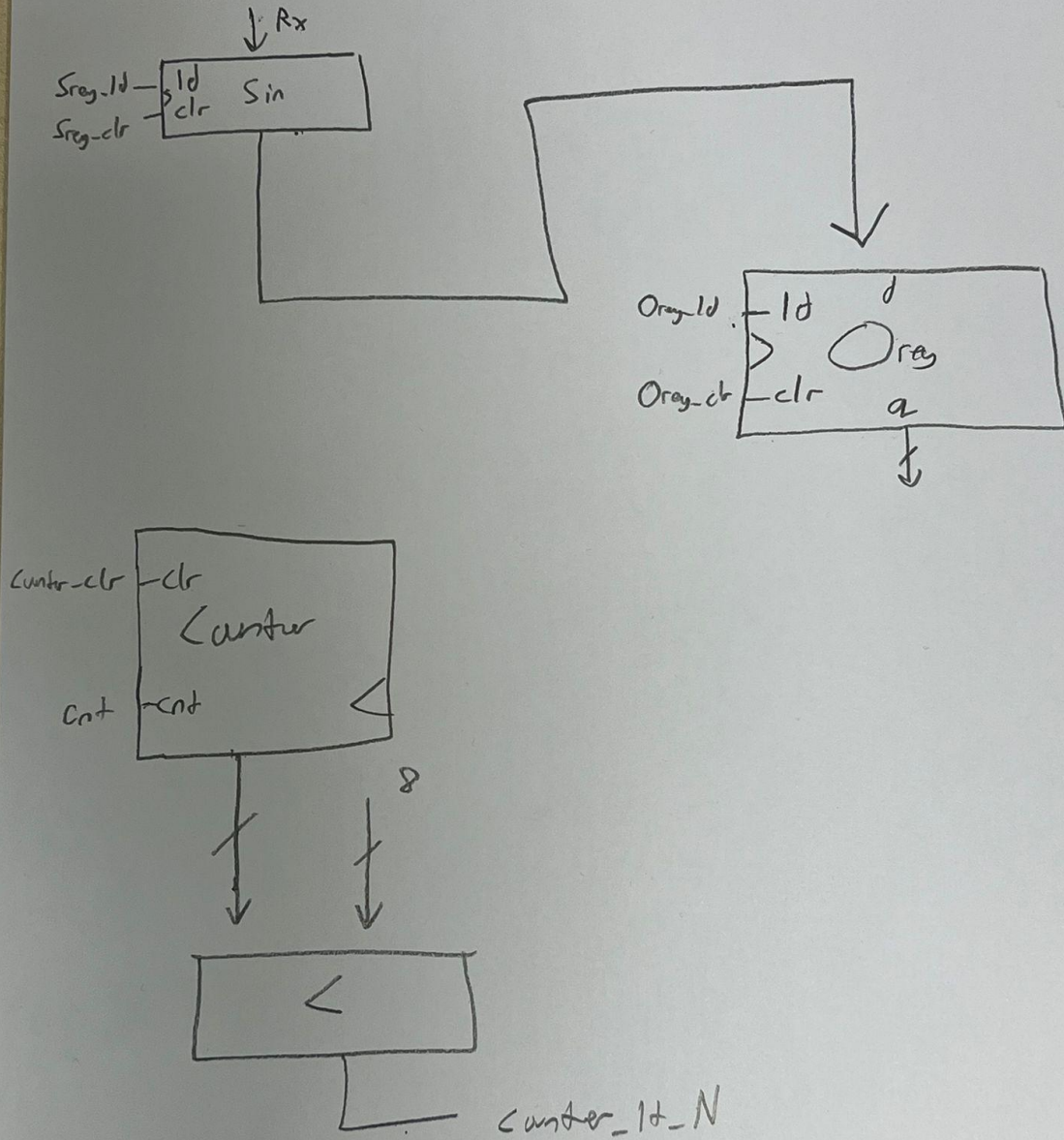

## Appendix

```
module Uart_st1(
    input logic BTNU, BTNL, BTNR, BTND, BTNC, clk_in, reset,
    input logic [7:0] d,
    output logic [7:0] q0,
    output logic [1:0] screen,
    output logic RorTx,
    output logic [3:0] Anode_Activate,
    output logic [6:0] LED_out
);

    reg [7:0] rxbuf [3:0];
    reg [7:0] txbuf [3:0];

    logic clk,tx;
    logic [7:0] q1;

    baudGenerator clockGenerator(clk_in,clk);
    transmitter_fsm trans(BTND,BTNC,clk,reset,d,q0,tx,txbuf);
    receiver_fsm receive(tx,clk,reset,q1,rxbuf);
    seven_segment_display
    displayer(BTNU,BTNL,BTNR,clk_in,reset,rxbuf,txbuf,screen,RorTx,Anode_Activate,L
    ED_out);
```

```
endmodule
```

```
module transmitter_fsm( input logic BTND, BTNC, clk,reset,
```

```
input logic [7:0] d , output logic [7:0] q0,
```

```
output logic tx, output reg [7:0] txbuf [3:0]);
```

```
    logic Treg_clr, Sreg_clr,q0, Counter_clr, Sreg_ld, Treg_ld, cnt, sout, counter_lt_8,  
Sreg_en;
```

```
    logic [1:0] s;
```

```
    logic [7:0] q1;
```

```
    eightBitRegister Treg(clk,Treg_clr,Treg_ld,d,q0);
```

```
    eightBitShiftRegister Sreg(clk,Sreg_clr,Sreg_ld,0,Sreg_en,txbuf[3],q1,sout);
```

```
    fourToOneMux frtOneMux(0,1,sout,0,s,tx);
```

```
    counter cntr(clk,Counter_clr,cnt,counter_lt_8);
```

```
    typedef enum logic [3:0] {S0,S1,S2,S3,S4,S5,S6,S7,S8} statetype;
```

```
    statetype [1:0] state, nextstate;
```

```
    always @(posedge clk, posedge reset)
```



```

if(reset) state <= S0;

else state <= nextstate;


//kuzeyyyyyyy

always_comb

case (state)

S0: nextstate=S1;

S1: begin

if(BTND) nextstate=S2;

else if(BTNC) nextstate=S4;

else nextstate=S1;

end

S2: nextstate=S3;

S3:

begin

if(BTNC) nextstate=S4;

else if(BTND) nextstate = S2;

else nextstate=S3;

end

S4: nextstate=S5;

S5: if(counter_lt_8) nextstate=S5;

else nextstate=S6;

S6: nextstate=S7;

S7: if(BTNC) nextstate=S7;

else nextstate = S1;

```

S8: if(BTND) nextstate=S8;

else nextstate = S1;

default: nextstate=S0;

endcase;

always @(state)

case (state)

S0: begin s= 2'b01; Treg\_clr=1; Treg\_ld =0; Sreg\_clr=1; Sreg\_ld=0; Sreg\_en=0;  
cnt=0; Counter\_clr=1; end

S1: begin s= 2'b01; Treg\_clr=0; Treg\_ld =0; Sreg\_clr=0; Sreg\_ld=0; Sreg\_en=0;  
cnt=0; Counter\_clr=0; end

S2: begin s= 2'b01; Treg\_clr=0; Treg\_ld =1; Sreg\_clr=0; Sreg\_ld=0; Sreg\_en=0;  
cnt=0; Counter\_clr=0; end

S3: begin s= 2'b01; Treg\_clr=0; Treg\_ld =0; Sreg\_clr=0; Sreg\_ld=0; Sreg\_en=0;  
cnt=0; Counter\_clr=0; end

S4: begin s= 2'b00; Treg\_clr=0; Treg\_ld =0; Sreg\_clr=0; Sreg\_ld=1; Sreg\_en=0;  
cnt=0; Counter\_clr=1; end

S5: begin s= 2'b10; Treg\_clr=0; Treg\_ld =0; Sreg\_clr=0; Sreg\_ld=0; Sreg\_en=1;  
cnt=1; Counter\_clr=0; end

S6: begin s= 2'b01; Treg\_clr=0; Treg\_ld =0; Sreg\_clr=0; Sreg\_ld=0; Sreg\_en=0;  
cnt=0; Counter\_clr=0; end

S7: begin s= 2'b01; Treg\_clr=0; Treg\_ld =0; Sreg\_clr=0; Sreg\_ld=0; Sreg\_en=0;  
cnt=0; Counter\_clr=0; end

S8: begin s= 2'b01; Treg\_clr=0; Treg\_ld =0; Sreg\_clr=0; Sreg\_ld=0; Sreg\_en=0;  
cnt=0; Counter\_clr=0; end

```
endcase
```

```
always_ff@(posedge clk)
```

```
if(state == S0) begin
```

```
txbuf[0] = 0;
```

```
txbuf[1] = 0;
```

```
txbuf[2] = 0;
```

```
txbuf[3] = 0;
```

```
end
```

```
else if (state == S2) begin
```

```
txbuf[0] <= q0;
```

```
txbuf[1] <= txbuf[0];
```

```
txbuf[2] <= txbuf[1];
```

```
txbuf[3] <= txbuf[2];
```

```
end
```

```
endmodule
```

```
module receiver_fsm( input logic rx,clk,reset,
```

```
    output logic [7:0] toDisplay,
```

```
    output reg [7:0] rxbuf [3:0]
```

```
);
```

```
    logic Oreg_clr, Sreg_clr, cnt, cnt_clr, Sreg_ld, Oreg_ld, counter_lt_8, Sreg_en,  
sout;
```

```
    logic [7:0] q0;
```

```
eightBitShiftRegister Sreg(clk,Sreg_clr,0,rx,Sreg_en,0,q0,sout);  
eightBitRegister Oreg(clk,Oreg_clr,Oreg_ld,rxbuf[3],toDisplay);  
counter cntr(clk,cnt_clr,cnt,counter_lt_8);
```

```
typedef enum logic [2:0] {S0,S1,S2,S3,S4,S5} statetype;  
statetype [1:0] state, nextstate;
```

```
always @(posedge clk, posedge reset)  
    if(reset) state <= S0;  
    else state <= nextstate;
```

```
always_comb  
case (state)  
    S0: nextstate = S1;  
    S1: if(rx) nextstate=S1;  
    else nextstate=S2;  
    S2: if(counter_lt_8) nextstate=S2;  
    else nextstate=S3;  
    S3: if(rx) nextstate=S4;  
    else nextstate=S0;  
    S4: if(rx) nextstate=S5;  
    else nextstate=S0;
```

```
S5: nextstate=S1;
```

```
default: nextstate=S0;
```

```
endcase
```

```
always @(state)
```

```
case (state)
```

```
S0: begin Oreg_clr = 1; Oreg_ld = 0; Sreg_clr = 1; Sreg_ld = 0; Sreg_en = 0;
```

```
cnt_clr = 1; cnt = 0;
```

```
end
```

```
S1: begin Oreg_clr = 0; Oreg_ld = 0; Sreg_clr = 1; Sreg_ld = 0; Sreg_en = 0;
```

```
cnt_clr = 1; cnt = 0; end
```

```
S2: begin Oreg_clr = 0; Oreg_ld = 0; Sreg_clr = 0; Sreg_ld = 0; Sreg_en = 1;
```

```
cnt_clr = 0; cnt = 1; end
```

```
S3: begin Oreg_clr = 0; Oreg_ld = 0; Sreg_clr = 0; Sreg_ld = 0; Sreg_en = 0;
```

```
cnt_clr = 0; cnt = 0; end
```

```
S4: begin Oreg_clr = 0; Oreg_ld = 0; Sreg_clr = 0; Sreg_ld = 0; Sreg_en = 0;
```

```
cnt_clr = 0; cnt = 0; end
```

```
S5: begin Oreg_clr = 0; Oreg_ld = 1; Sreg_clr = 0; Sreg_ld = 0; Sreg_en = 0;
```

```
cnt_clr = 0; cnt = 0; end
```

```
endcase
```

```
module seven_segment_display(
```

```
input logic BTNU, BTNL, BTNR, clk, reset,
```

```
input logic [7:0] rxbuf [3:0],  
input logic [7:0] txbuf [3:0],  
output logic [1:0] screen ,  
output logic RorTx,  
output logic [3:0] Anode_Activate,  
output logic [6:0] LED_out  
);
```

```
reg [7:0] display_buf [3:0];  
reg [1:0] current_digit;  
reg [1:0] array_index;  
reg [3:0] BCD;  
reg [19:0] refresh_counter;  
wire [1:0] LED_activating_counter;  
reg display_rxbuf;
```

```
// Refresh counter for multiplexing display digits
```

```
always @(posedge clk, posedge reset) begin
```

```
    if(reset) begin
```

```
        refresh_counter <= 0;
```

```
        RorTx <= 0;
```

```
    end else begin
```

```
        refresh_counter <= refresh_counter + 1;
```

```
    end
```

```
end
```

```
assign LED_activating_counter = refresh_counter[19:18];
```

```
always_ff@(posedge clk, posedge reset) begin
```

```
    if(reset) begin
```

```
        display_buf <= txbuf;
```

```
        current_digit <= 0;
```

```
        array_index <= 0;
```

```
    end
```

```
    else if(BTNU) begin
```

```
        RorTx <= ~RorTx;
```

```
        display_buf <= RorTx ? rxbuf : txbuf;
```

```
    end
```

```
    else if(BTNL) begin
```

```
        array_index <= (array_index == 0) ? 3 : array_index - 1;
```

```
    end
```

```
    else if(BTNR) begin
```

```
        array_index <= (array_index == 3) ? 0 : array_index + 1;
```

```
    end
```

```
end
```

```
// Determine which digit to activate and display
```

```
always @(*) begin
```

```
    case(LED_activating_counter)
```

```
        2'b00: Anode_Activate <= 4'b1110;
```

```
        2'b01: Anode_Activate <= 4'b1101;
```



```

        2'b10: Anode_Activate <= 4'b1011;

        2'b11: Anode_Activate <= 4'b0111;

    endcase

    BCD <= display_buf[array_index][3:0];

end

always @(*) begin

    case(BCD)

        4'b0000: LED_out = 7'b0000001; // Example pattern for '0'

        4'b0001: LED_out = 7'b1001111; // "1"

        4'b0010: LED_out = 7'b0010010; // "2"

        4'b0011: LED_out = 7'b0000110; // "3"

        4'b0100: LED_out = 7'b1001100; // "4"

        4'b0101: LED_out = 7'b0100100; // "5"

        4'b0110: LED_out = 7'b0100000; // "6"

        4'b0111: LED_out = 7'b0001111; // "7"

        4'b1000: LED_out = 7'b0000000; // "8"

        4'b1001: LED_out = 7'b0000100; // "9"

        4'b1010: LED_out = 7'b0001000; // "A"

        4'b1011: LED_out = 7'b0000011; // "B"

        4'b1100: LED_out = 7'b1000110; // "C"

        4'b1101: LED_out = 7'b0100001; // "D"

        4'b1110: LED_out = 7'b0000110; // "E"

        4'b1111: LED_out = 7'b0001110; // "F"

        default: LED_out = 7'b1111111; // Blank
    endcase
end

```

```
        endcase
```

```
    end
```

```
    assign screen = (array_index < 2) ? 2'b01 : 2'b10;
```

```
endmodule
```

```
module baudGenerator#(parameter N = 112500)(input logic clk_in,
```

```
        output logic clk);
```

```
    reg [32:0] counter;
```

```
    reg clk_out = 0;
```

```
    always@(posedge clk_in)
```

```
    begin
```

```
        counter <= counter+1;
```

```
        if(counter == 150000000/N)
```

```
        begin
```

```
            counter <= 0;
```

```
            clk_out = ~clk_out;
```

```
        end
```

```
    end
```

```
assign clk = clk_out;
```

endmodule